

## **INJECTION-PERIOD METER**

### **IPM10**

**If you do not intend to build an IPE-GP or IPE-GS** but still want to measure opening time for fuel injectors - this circuit may be useful? With IPM10 one gets accurate information about pulse width whether indoors or on the field. Usually the opening time at idle is what is of interest, therefore this circuit not measure longer than maximum 13 milliseconds. The measurement range is 0.5-10mS with high accuracy. At idle: times over 5 mS are rare - so for extra high accuracy one should calibrate IPM10 for 0.5-7mS because the linearity is then higher.

#### *Luxorparts - Digital Voltage Meter*




**The construction is a bit special** when I chose to use a current-saving voltage meter from *Kjell & Company* (powered by 3-30V and measure up to 99V) to digitally deliver the actual pulse time, which is then presented as a volt value (by one decimal) instead - on this way, the design of the electronics for the display circuit has been skipped, which has simplified the construction considerably. Since the voltage of a car in operation is at least 14 volts, it is theoretical to measure up to 12.5 mS (depends on the selected Op).

*Before this creation began to take shape I tested an automotive multimeter from Biltema, with the ability to measure injector time but it did not work well. The K&C Display Meter powered by IPM10 can be placed in the passenger compartment fed with a USB cable, which could actually intend to be used for an RCW module to IPE-GS? Two poles/wires and one ground (the screening on the USB cable) are what it takes to communicate with an IPM10. For example, the two remaining poles can be used by two LEDs belonging to a LFFGM or other modules? Or, IPM10 is a complement to any pulse extender of any kind.*

**The device is based on the logic IC: 4066**, which is equipped with four analogue gates. Such a gate is necessary for the "sample and hold" function but it is also possible to connect them as inverting gate elements which means that one do not need to use more than one logic integrated circuit here. A voltage reference (here 8 volts) is necessary so that the measured values do not assume different values depending on the power supply voltage.

*IPM10 measures all pulses but ignores interference and/or spikes. It is necessary because an IPE-Gx generates a spike, which then not affects the measurement.*


# CIRCUIT DIAGRAM

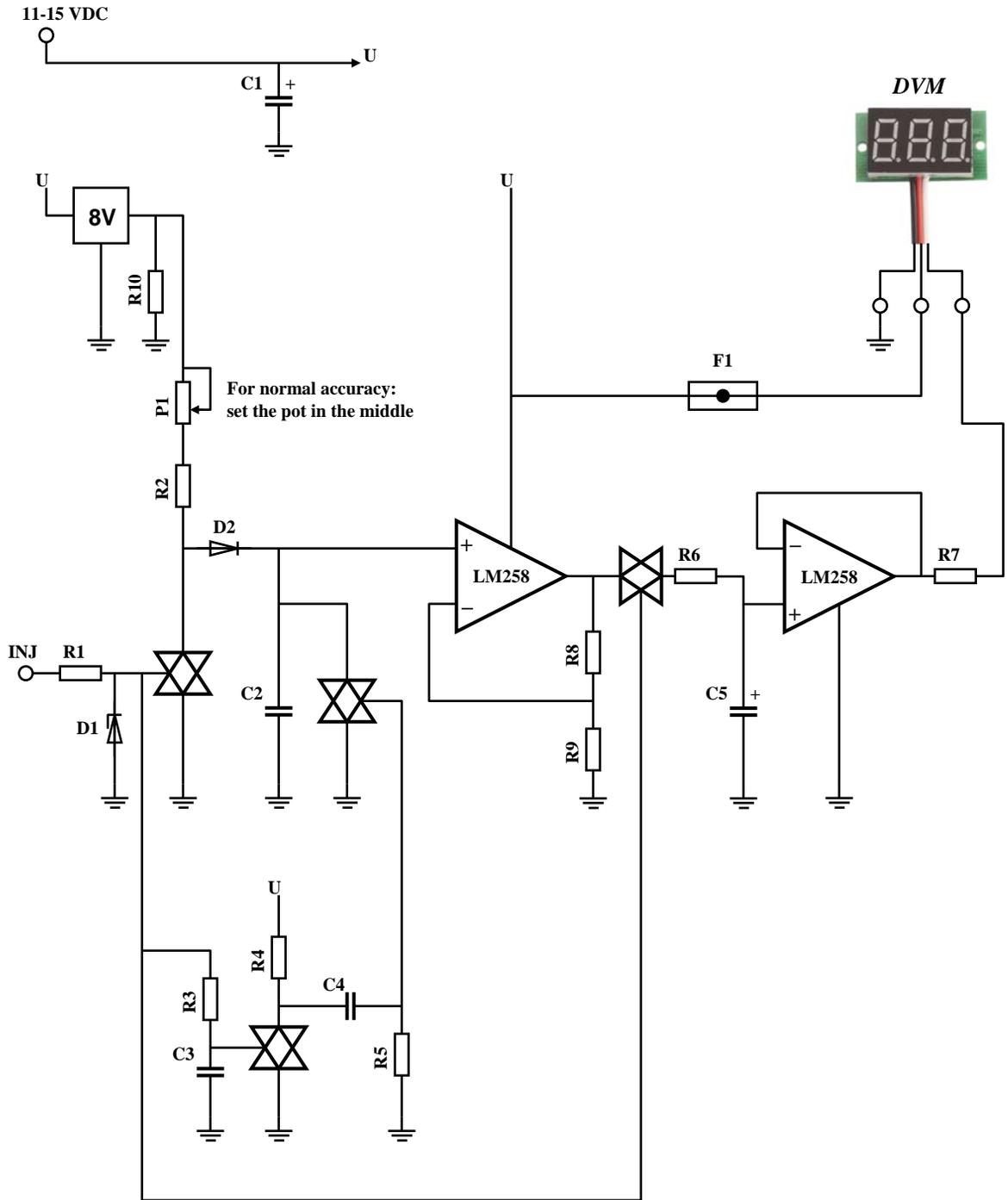

*IPM10 resists both cold and heat without measurement errors occur. The display unit starts to show error round about -10 C. It can however resist heat well.*

<b>PROJECT</b>	Injection-period Meter	
<b>MODULE</b>		
<b>MODEL</b>	IPM10	
<b>AUDIT</b>	A-1	<b>DRAWING: 1 of 1</b>
<b>SUPPLY</b>	11-15 VDC	
<b>CURRENT</b>	Max 22mA	
<b>OTHER</b>		
	B. Lindqvist	

# PLACING OF COMPONENTS

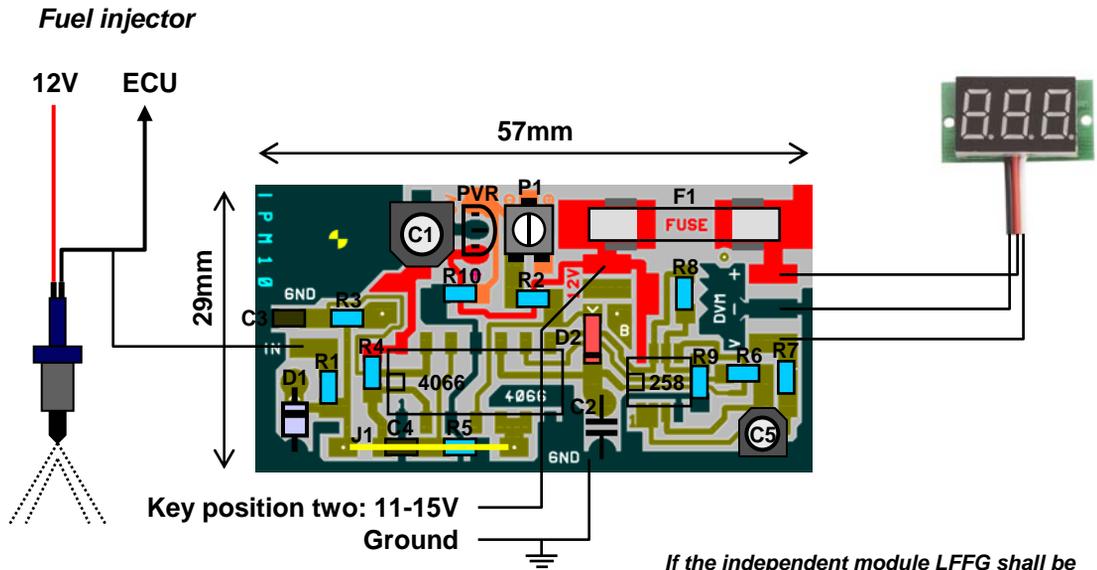

If the independent module LFFG shall be combining with this circuit so can it be powered by 8V from IPM10. The aforementioned can use a double sided board if they will coexist, because they have same dimensions.

### SMR1206:

- R1 = 2k2
- R2 = 510k
- R3 = 100k
- R4 = 6k8
- R5 = 68k
- R6 = 10k
- R7 = 220Ω
- R8 = 100k
- R9 = 6k8
- R10 = 1k5

### SMC1206:

- C3 = 220p
- C4 = 1n

### Other components:

- C1 = 47uF , 16V , E-lytic , SMD / hole mount
- C5 = 10uF , 16V , E-lytic , SMD / hole mount
- C2 = 220n , plastic , hole mount
- P1 = 100k , chiptrimpot , 23B , SMD
- F1 = 500mA , melting fuse
- J1 = Jumper


### Semiconductors:

- D1 = 12V , zener diode , ≥ 0.5W , hole mount
- D2 = BAS32 , SMD
- PVR = 8V , positive voltage regulator , hole mount
- 4066 = Quad bilateral switches , hole mount
- LM258 = Low power dual operational amplifiers , SMD
- LM2904 is a better chose then LM258!*

The circuit requires only a single side board. All components should be handled as SMD, thus made, all soldering take place on the same side. Holes can be drilled for the M3-screw and J1.


PROJECT	Injection-period Meter	
MODULE		
MODEL	IPM10	
AUDIT	A-1	DRAWING: 1 of 1
OTHER		
B. Lindqvist		2017-06
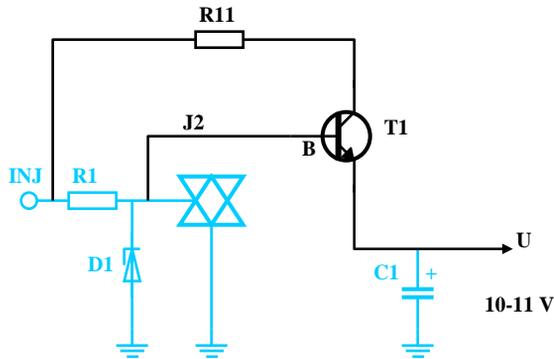
## CIRCUIT DIAGRAM AND PLACING OF COMPONENTS



There is a possibility that IPM10 will provide itself through the fuel injector it currently measures. Then one not need any supply voltage from the outside.

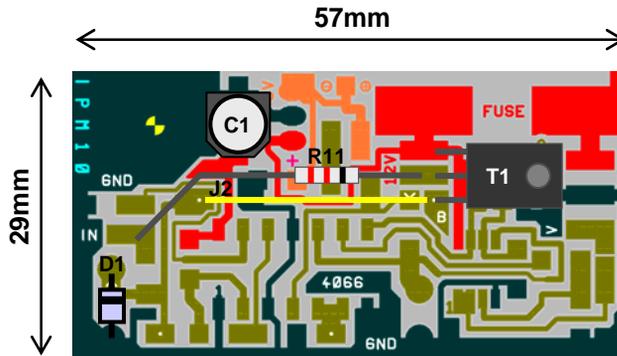If one choose this method, one can expect a slightly lower voltage and thus a smaller measuring range (0-10 mS).



Only components required for self-providing are deployed.

### Components:

T1 = BD439 or similar NPN , hole mount

R11 = 22Ω , hole mount

J2 = Jumper (to base on T1)

### Components that shall be changes:

C1 ≥ 220uF , 16V , E-lytic , SMD / hole mount

D1 = 13V , zener diode , ≥ 0.5W , hole mount



The circuit requires only a single side board. All components should be handled as SMD, thus made, all soldering take place on the same side. Holes can be drilled for the M3-screw, J1 and J2.

PROJECT	Injection-period Meter	
MODULE		
MODEL	IPM10	
AUDIT	A-1	DRAWING: 1 of 1
OTHER	No supply	
B. Lindqvist		2017-06

## MODULE PLACING OF COMPONENTS AND CIRCUIT DIAGRAM

The function of this module is only to increase the readability on the display when the engine is off or in case of engine brake.

Additional electronics is demanded if a reset of IPM10 shall be possible. The OP amplifiers tend to add voltage when the INJ input is static high or low. Z forces down the second OP + input when no pulses are generated from the injector.

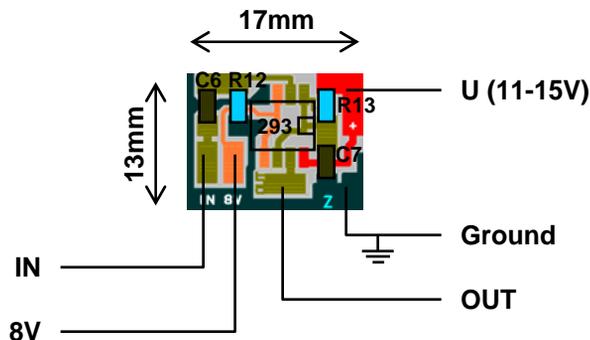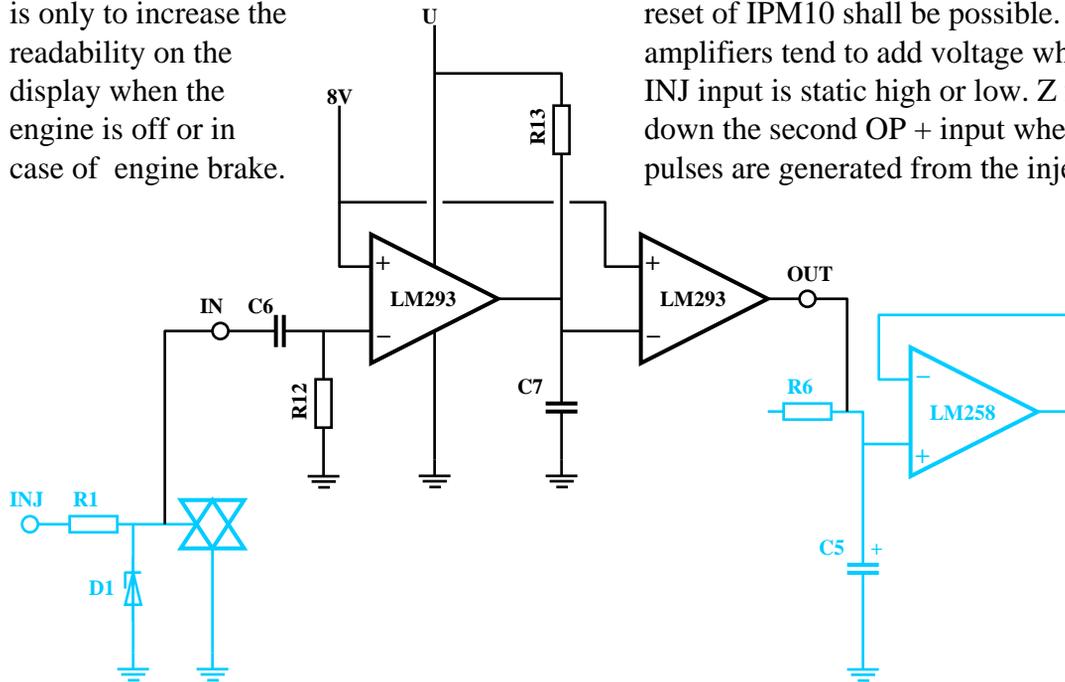

**SMR1206:**  
R12 = 1M  
R13 = 4M7

**SMC1206:**  
C6 = 220p  
C7 = 100n


**IC:**  
LM293 = Low power dual voltage comp , SMD  
*LM2903 is a better chose then LM293!*

The circuit requires only a single side board. All components is of the type SMD.

PROJECT	Injection-period Meter	
MODULE	Zero	
MODEL	Z	
AUDIT	A-1	DRAWING: 1 of 1
OTHER	For resetting DVM	
B. Lindqvist		2017-06
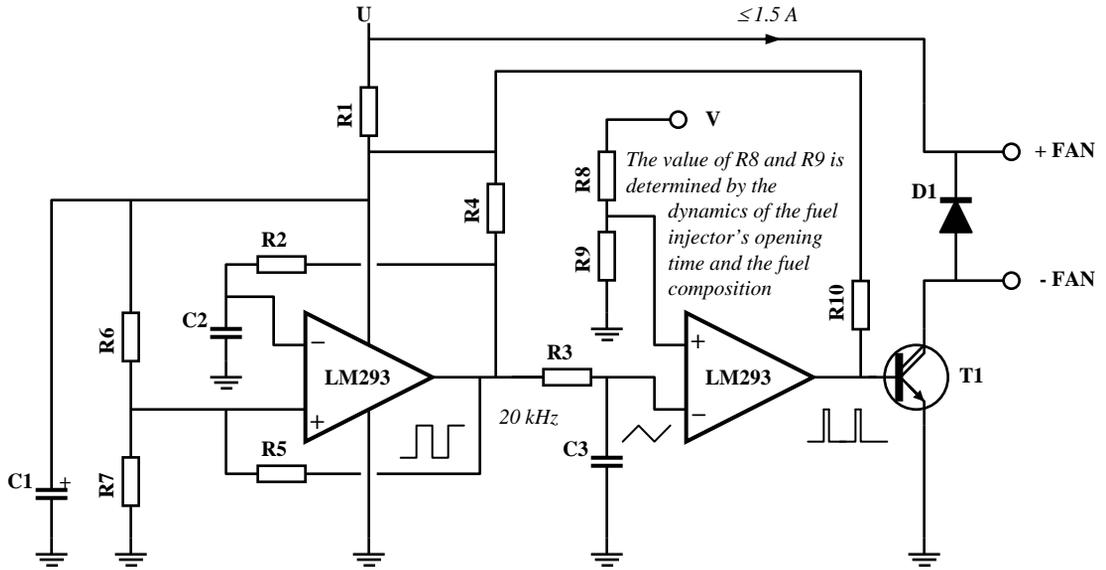
## MODULE PLACING OF COMPONENTS AND CIRCUIT DIAGRAM

The step is not far letting IPM10 controls the speed of a 12V PC fan. This fan should be placed at the engine's intake to provide more efficient air supply. This may be similar to a primitive air compressor (that lack the inertia a turbocharger has). What is missing is a PWM circuit that effectively minimizes heat loss.



### SMR1206:

R1 = 47Ω  
 R2 = 33k  
 R3 = 100k  
 R4 = 4k7  
 R5 = 100k  
 R6 = 100k  
 R7 = 100k  
 R8 = ?  
 R9 ≥ 100k  
 R10 = 4k7

### SMC1206:

C2 = 1n  
 C3 = 150p

### Other components:


C1 = 22uF , 16V , E-lytic , SMD / hole mount

D1 = 1N4937 , ultrafast diode , hole mount

T1 = BD677 , Darlington transistor , hole mount

LM293 = Low power dual voltage comp , SMD


**LM2903 is a better chose then LM293!**

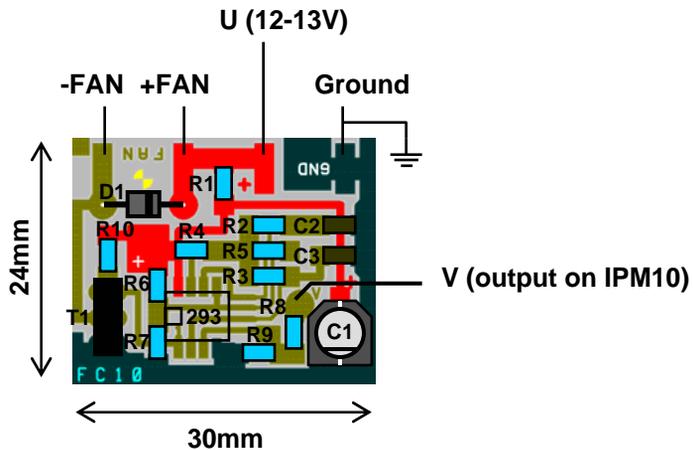

The circuit requires only a single side board. All components should be handled as SMD, thus made, all soldering take place on the same side.

PROJECT	Injection-period Meter	
MODULE	Fan Control	
MODEL	FC10	
AUDIT	A-2	DRAWING: 1 of 1
OTHER	Controlling fan speed	
B. Lindqvist		2017-08

PHOTOS

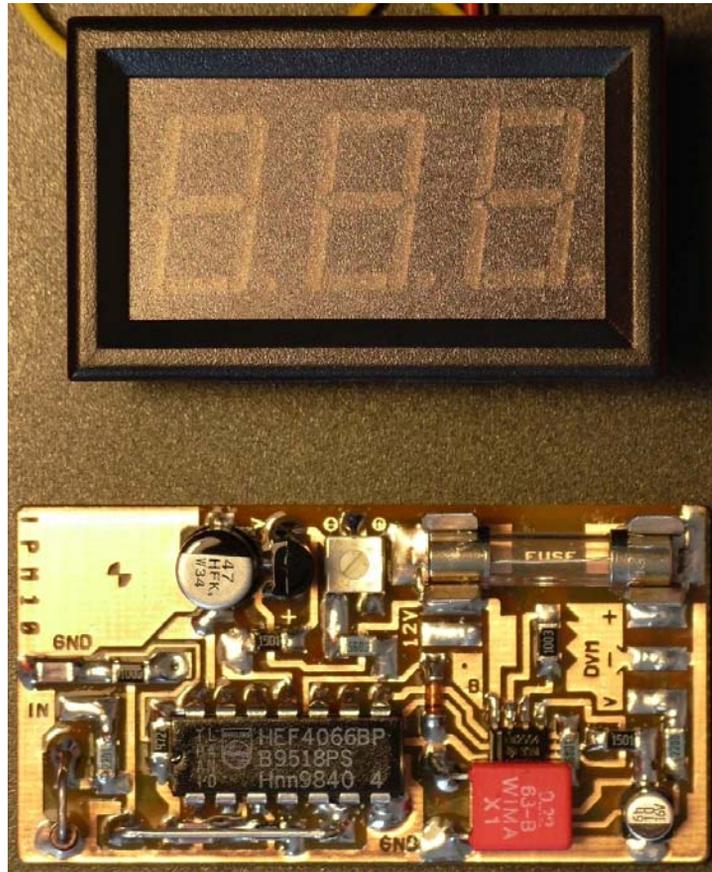

IPM10 under a DVM

