

SMART SENSOR CIRCUIT

SSC

Many who have converted their gasoline cars to E85 will usually manipulate the engine temperature sensor and in that way (try to) fool the car's electronic control unit (E85 makes a cooled car engine harder to start). **I will now present a proven methodology:**

The problem is that alcohol-based fuels do not contribute at any help when the engine is cold and shall be started. Unlike other liquid fuels such as gasoline are alcohols often difficult to gasify, particularly at low temperatures. One simply has to increase the fuel supply so that the active sub-component (gasoline) can be supplied in abundant quantities.

Actually it is not so smart to trim a (cold) spark-ignition engine to thereby get it to start/run normally because the alcohol component is not ready to participate in propulsion - instead it gets lost. It is not only during the start of the engine that requires extra fuel - while the engine is about to heat up must additional fuel/alcohol be added.


Anyway, we will assume that you still wish to manipulate the temperature sensor, thus the temperature sensor located on the engine block. There are also other temperature sensors on a vehicle such as in the air channel, but this sensor is mainly used to calculate the proper quantity of air and contributes (current the fuel quantity) to a lesser extent than the engine sensor. So, if one fool the sensor on the engine block that it is colder than it actually is, will it inevitably result to an increased fuel quantity.

SSC is intelligent into the account the number of parts. With 6 components will one get a circuit that working down to +30°F and not only just start a cold engine (choke), but also - after that - boost the input fuel during the engine warm-up phase. It diminishes then gradually and ceases completely when the engine is adapted to alcohol. This can SSC do and it is the resistor R2 that determines the delay of this decreasing function.


Resistor R3 can be said; smooths extreme situations. If an engine already is warm when it starts, so will it means that the temperature sensor's resistance also is low. When SSC choke the engine (which it always does after a long electric break / downtime) will the sensor resistance plays an important role - is it low will although the voltage across the sensor stay low. The output of the SSC will always depend to some extent by the temperature sensor's resistance.

SSC works almost exclusively with time unless you choose to build the complement circuit - then extend the number of components to six and SSC can operates over an infinite range of temperatures. SSC can then be fed with 12V (instead of 5V) and below 20°F will the supply voltage stepping up to one volt (to 6 volts). In addition, there are a host of other selections for various features and options - maybe you even can convert your car with this concept? SSC does not require that one need to break up existing electronics / cables - just connect it to the temperature sensor warm side. The sensor must be grounded!

CIRCUIT DIAGRAM

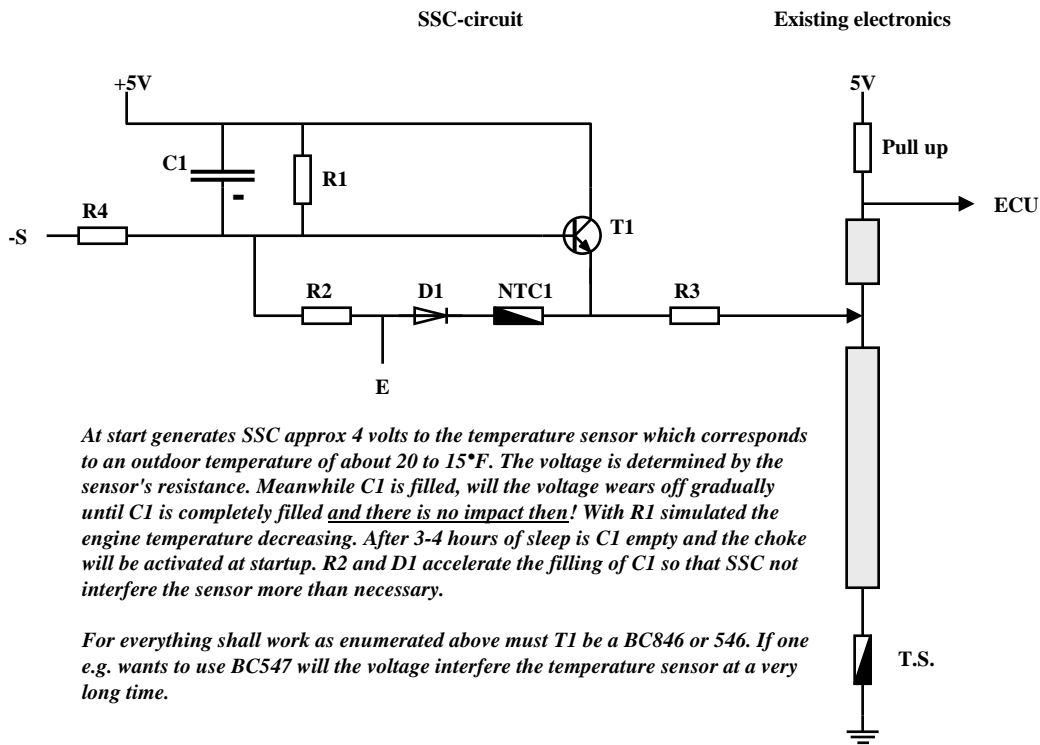


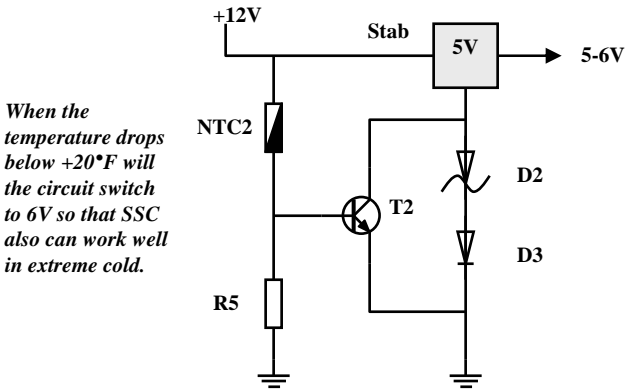Temperature adjustment circuit
(complement)




Switch circuit for turning off
(optional)

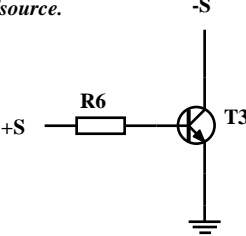Allows use of switches or via a voltage pulse from some other device/source.




A switch in the cabin
(optional)

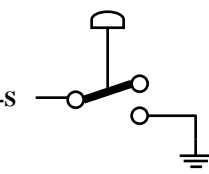If one pulls a switch into the cabin can one choose when and how much SSC shall be active.




PROJECT	Smart Sensor Circuit		
MODULE			
MODEL	SSC		
AUDIT	A-2	DRAWING: 1 of 2	
SUPPLY			
CURRENT			
OTHER	Tested		
B. Lindqvist			2012-06

CIRCUIT DIAGRAM

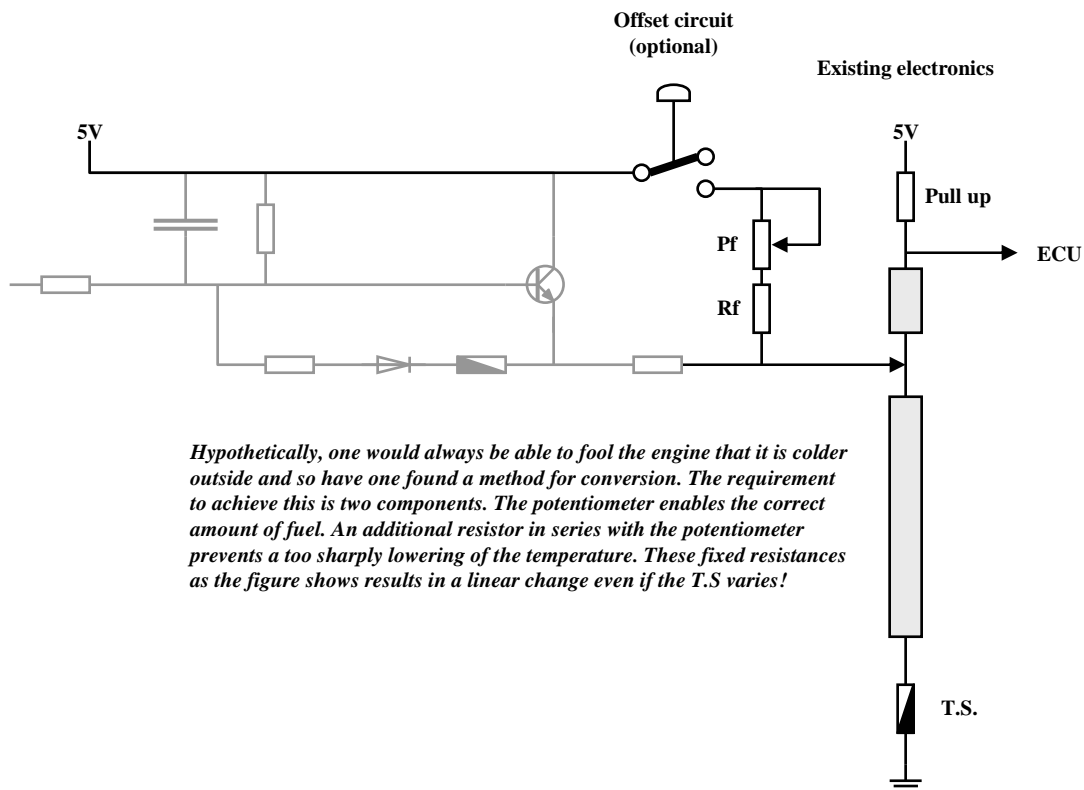

Control module - RCW1 (optional)

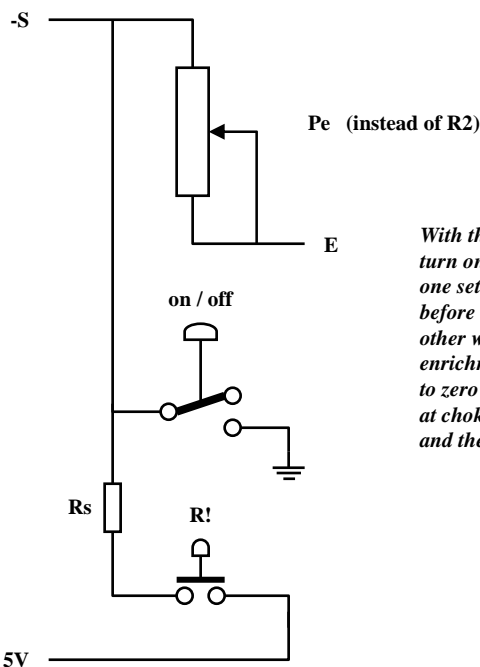


With this module can one remotely turn on or off SSC. With Pe can one set how long it takes before C1 becomes filled or in other words: How long the extra enrichment will last. If one turn Pe to zero becomes only a short-pulse at choke. "R" restores both choke and the enrichment time.

SAM



RCW1 is now prepared also working with SAM. Pe should then be replaced by P21 (50k). At two places on the layout shall the copper track be sanded off. "E" is connected to R21 and the other two against each contact point P21 occupies. A cable with 6 poles are required if all control functions is selected to be available according to the schedule.

PROJECT	Smart Sensor Circuit	
MODULE		
MODEL	SSC	
AUDIT	A-2	DRAWING: 2 of 2
SUPPLY		
CURRENT		
OTHER		
B. Lindqvist		2012-11


PLACING OF COMPONENTS

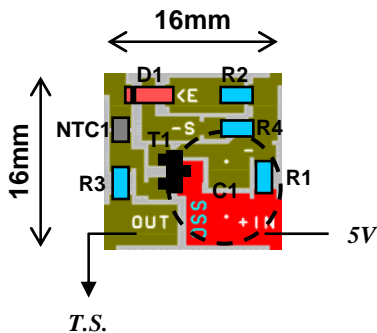

RCWI

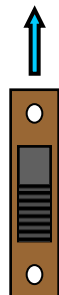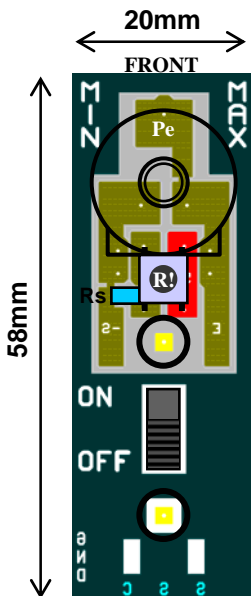

Single side board. All components are surface mounted except C1, Pe and switches. C1 can be an SMD-capacitor. Drill hole for C1, Pe, switches and the strap.

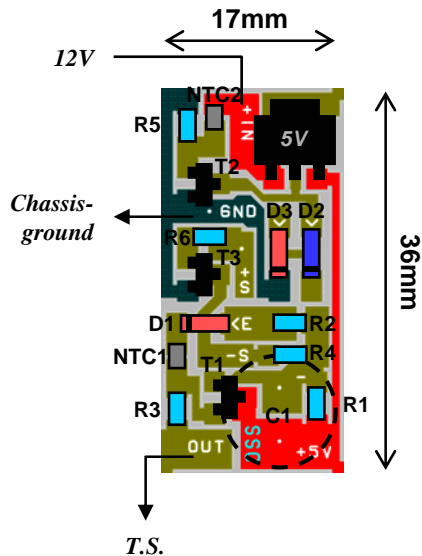

SMR1206:

R1 = 10M

R2 = 0-220k (82k if NTC1 is used)

R3 = 220Ω if T.S. ≈ 1k

If T.S. ≈ 2k shall R3 = 470Ω - also cut R2 in half!

R4 = 100-500Ω (optional)

R5 = 820Ω (complement)

R6 = 22k (optional)

Other components:

C1 = 470μ, E-lytic Hole/SMD

D1 = BAS32 (1N4148), SMD

D2 = BAS85 (BAT85), SMD (complement)

D3 = BAS32 (1N4148), SMD (complement)

T1 = BC846B (BC546B), SMD

T2 = BC847B (BC547B), SMD (complement)

T3 = BC847B (BC547B), SMD (optional)

NTC1 = 10k at 25°C, SMD (can be excluded)

NTC2 = 4k7 at 25°C, SMD (complement)

The Stab = LM340MP, 5V, SMD (complement)

Pe = 100k, PT-15NV(17), hole mount

Also PT-10 / PTC-10

Rs = 220Ω, SMD

Switch = Elfa: 35-111-82


R! = TACT-Switch, compact snap-in type




PROJECT	Smart Sensor Circuit		
MODULE			
MODEL	SSC		
AUDIT	A-2	DRAWING: 1 of 1	
OTHER	Tested		
B. Lindqvist		2012-11	

MODULE PLACING OF COMPONENTS AND CIRCUIT DIAGRAM

During the spring, summer and fall when the temperature is around 40 degrees or higher, it happens that the idle becomes too high after a cold start. The reason is because SSC keeps the voltage across the T.S although that the choke has done its job and not serves any purpose anymore. SAM allows the choke to work undisturbed but will then begins to turn down the voltage pretty soon, while the idle gets a lower speed - then it stops and SAM allows the enrichment phase proceeds in a customary manner. SAM copy the engine temperature sensor and it will corresponds to a standard K220 type of sensor. The emulation allows obtaining adjacent values of the circuit that suppresses the voltage from SSC. The design also contains a temperature-controlled accelerator, current the enrichment when it's hot out there - it's the lower comparator that controls this function. With SAM shall SSC preferably be located in the cabin but in an inconspicuous place. It is only during cold starts that SAM affects the idle, is the engine already warm (engine heater) causes a high idle no wear. Besides idling reduction, affects P21 the enrichment period and choke. A MAX set P21 does not lead to any idle reduction but the time and choke will be at a maximum - reverse means; large idle reduction while the time and choke becomes minimal. Start from the middle point and adjust until the idle, time and choke is acceptable.

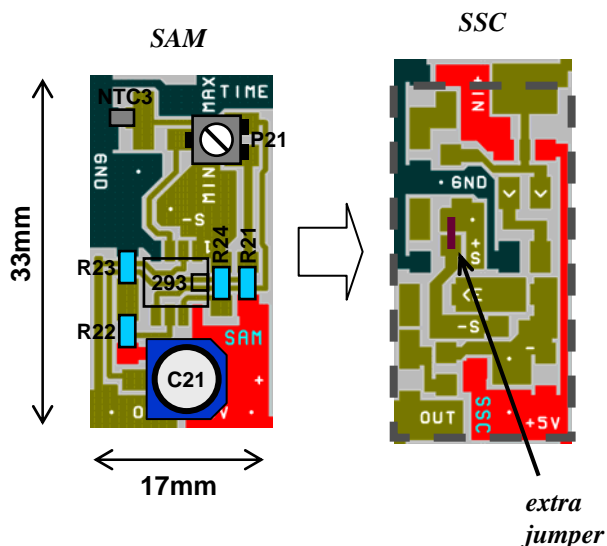

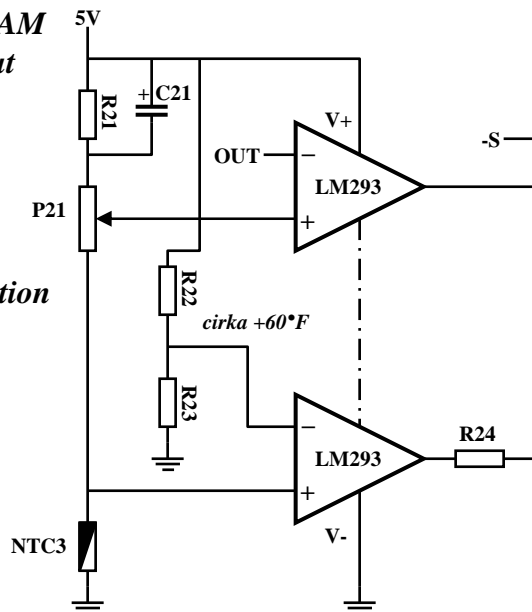Single side board. All components are surface mounted. The four holes connecting SAM with SSC by wires. SAM is placed over SSC and is soldered via said contact points. Selected SAM_GP shall SAM be etched on the bottom of SSC2 and then requires a double side board!



Components:

R21 = 47k , SMD 1206
 R22 = 22k , SMD 1206
 R23 = 33k , SMD 1206
 R24 = 1M5 if R3 = 220Ω , SMD
 R24 = 680k if R3 = 470Ω , SMD
 P21 = 50k , 23A/B , SMD
 C21 = 220μ , E-lytic SMD
 NTC3 = 100k at 25°C , SMD
 LM293 = Dual comparator , SMD

NOTE:

If R3 = 220Ω becomes R2 = 220k
 If R3 = 470Ω becomes R2 = 100k

PROJECT	Smart Sensor Circuit	
MODULE	Smart adjustment module	
MODEL	SAM	
AUDIT	A-2	DRAWING: 1 of 1
OTHER	Tested	
B. Lindqvist		2012-11

RCW2

Front View: Dimensions 20mm (width) and 58mm (height). Components include a fuel gauge (Pf), a potentiometer (Rf), a switch (R!), a USB port, and a fuel amount indicator.

Top View: Dimensions 17mm (width) and 54mm (height). Components include a USB port, a potentiometer (Pe), a switch (R!), and a fuel amount indicator. Wire jumpers are shown connecting the USB port to the potentiometer.

Circuit Diagram: Shows the electrical connections for the fuel amount and enrichment time. The fuel amount circuit includes a 5V supply, a potentiometer (Pf), a resistor (Rf), and an output (OUT). The enrichment time circuit includes a -S supply, a potentiometer (Pe), a switch (R!), and an output (E).

Components:

- Pf = 100k , PT-15NV(17) , hole mount
- Also PT-10 / PTC-10
- Rf = 1-3k (= "pull up") , SMD
- Pe = 100k , 72PT , hole mount
- USB = USBA and USBB , PCB
- R! = TACT-Switch, compact snap-in type

Notes:

- If one draw out the module from the USB-cable will the offset-function stop but SSC is still active!
- Turn off the unit through unplugging it or with a switch between R3 and T.S.

Table:

PROJECT	Smart Sensor Circuit		
MODULE	Remote control by wire		
MODEL	RCW2		
AUDIT	A-2	DRAWING: 1 of 1	
OTHER	Hypothetic!		
B. Lindqvist		2012-06	


This module require a double side board and a number of holes must be drilled, since it contain both surface- and hole mount components.

PROJECT	<i>Smart Sensor Circuit</i>	
MODULE	<i>Remote control by wire</i>	
MODEL	RCW2	
AUDIT	A-2	DRAWING: 1 of 1
OTHER	<i>Hypothetical!</i>	
<i>B. Lindqvist</i>		<i>2012-06</i>

PHOTOS




SSC base circuit (earlier prototype)

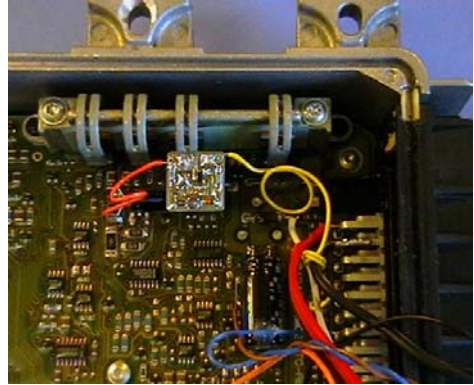


in a ECU



With the complement circuit

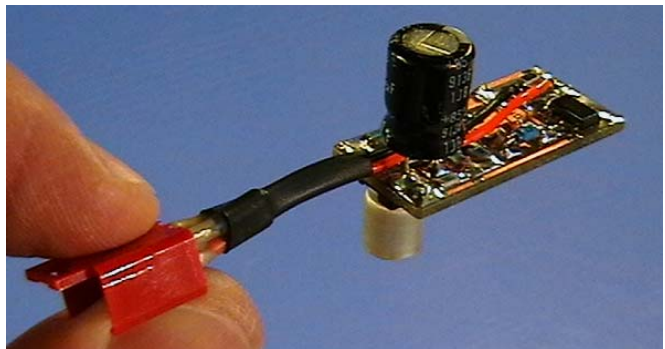

SSC (ready to plug) with SAM included

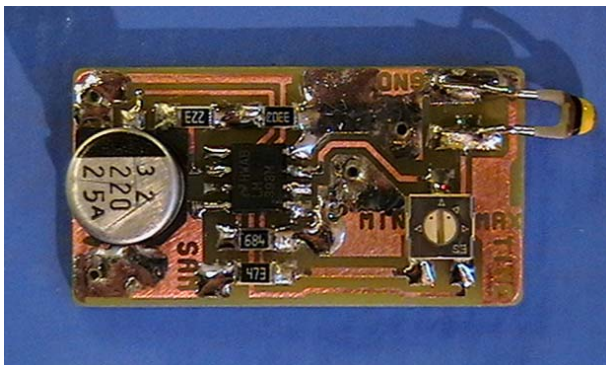

SAM



RCWI